

# **Title : Single Phase Transformers**

Date: 23/03/2020

Name of Faculty: Ms. Richa Dubey


Lecture No : 06

Source of information : B. L. Theraja, “Electrical Technology – Part I and II”, S. Chand and Co. 2012

Page no.


---

# Cut view of transformer

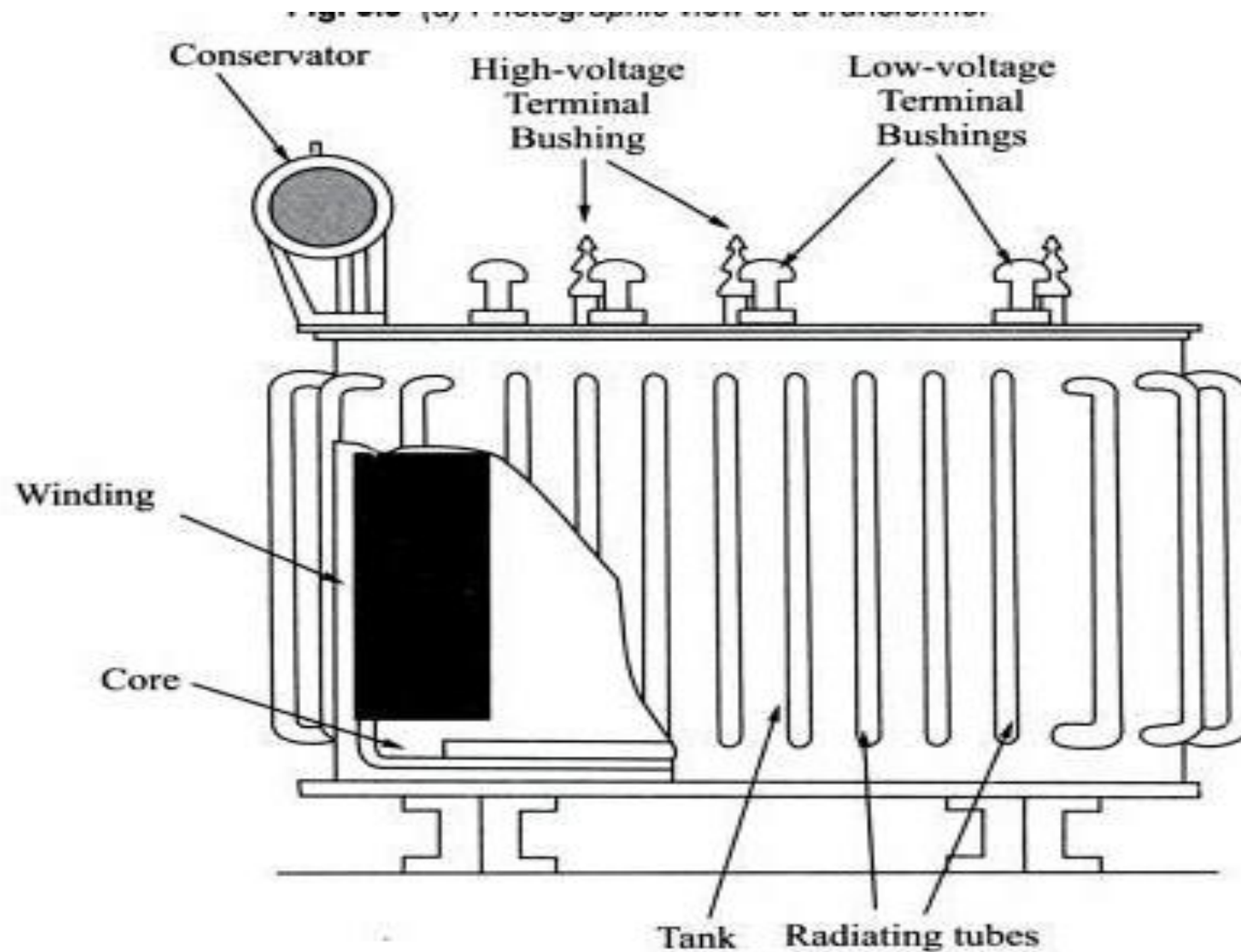


# Transformer with conservator and breather

---

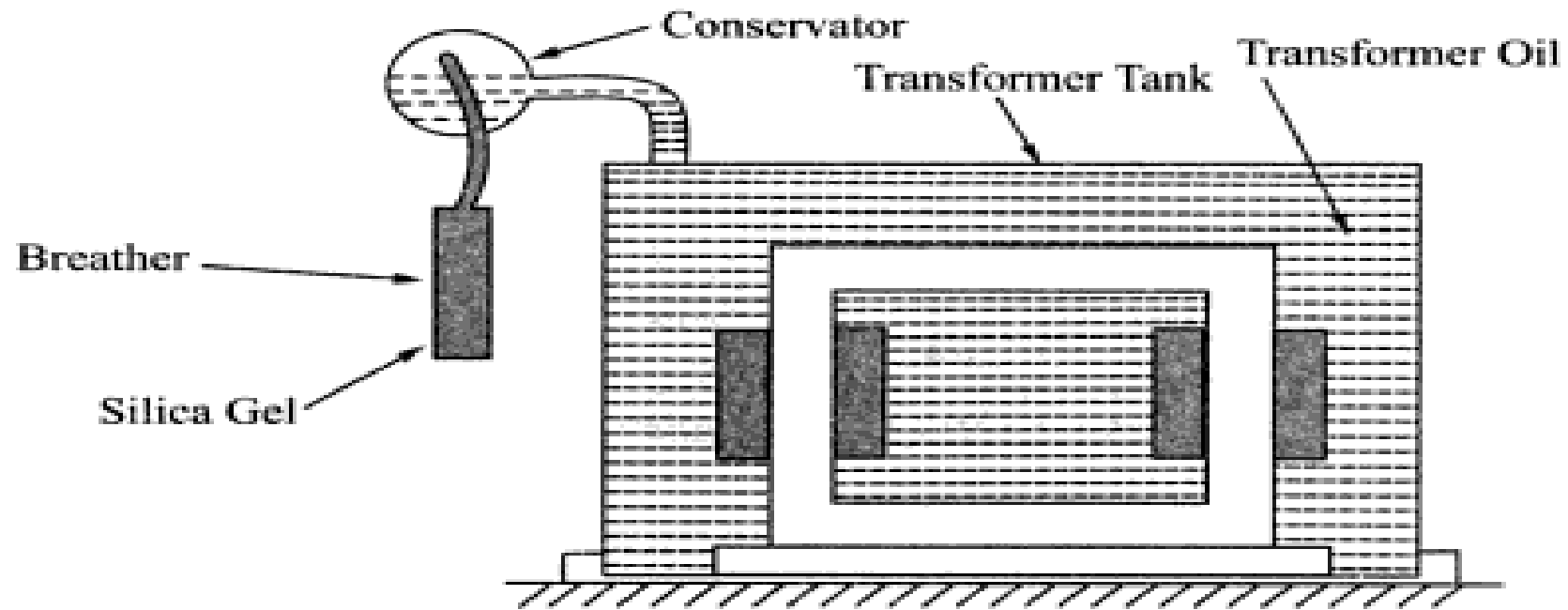

# Working of a transformer

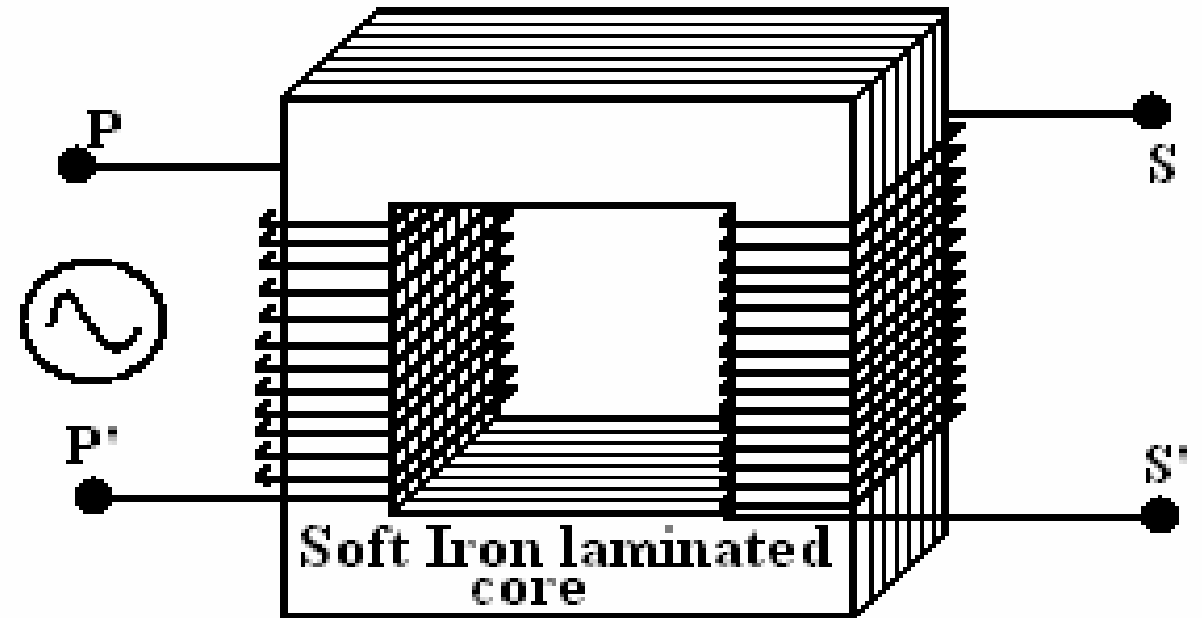1. When current in the primary coil changes being alternating in nature, a changing magnetic field is produced
2. This changing magnetic field gets associated with the secondary through the soft iron core
3. Hence magnetic flux linked with the secondary coil changes.
4. Which induces e.m.f. in the secondary.



# Single Phase Transformer

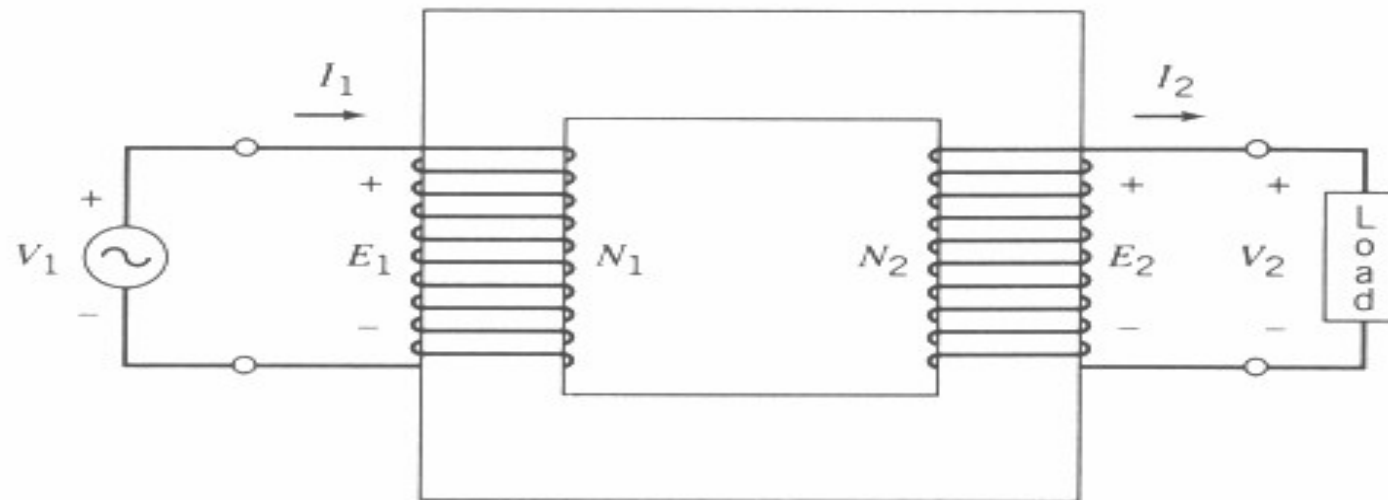


FIGURE 4.8 A transformer circuit.

- A single phase transformer
  - Two or more winding, coupled by a common magnetic core

# Ideal Transformers

## **Zero leakage flux:**

~~- Fluxes produced by the primary and secondary currents are confined within the core~~

## **The windings have no resistance:**

- Induced voltages equal applied voltages



## **The core has infinite permeability**

- Reluctance of the core is zero
- Negligible current is required to establish magnetic flux

## **Loss-less magnetic core**

- No hysteresis or eddy currents

# Ideal transformer

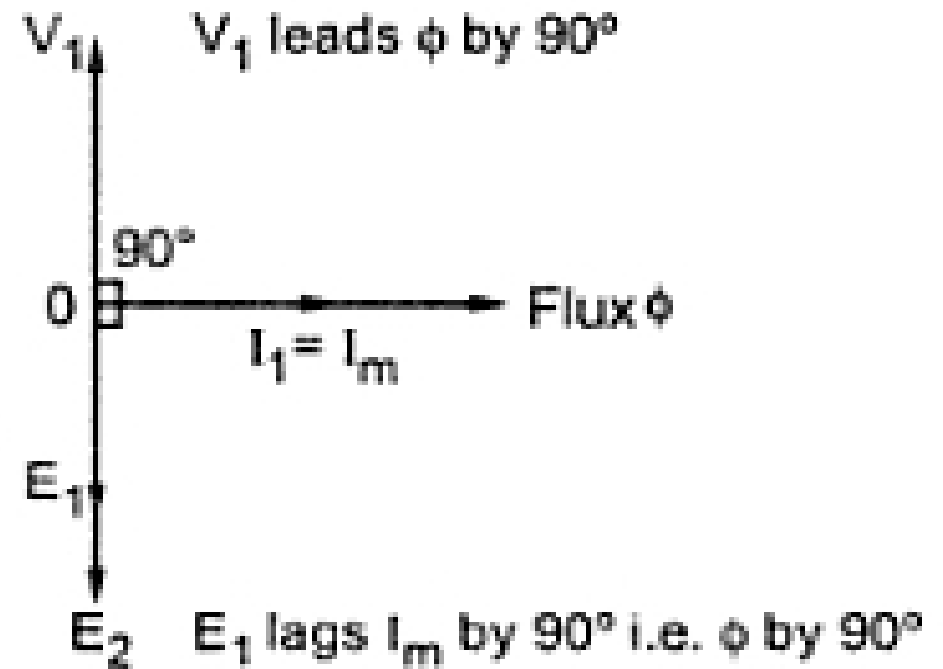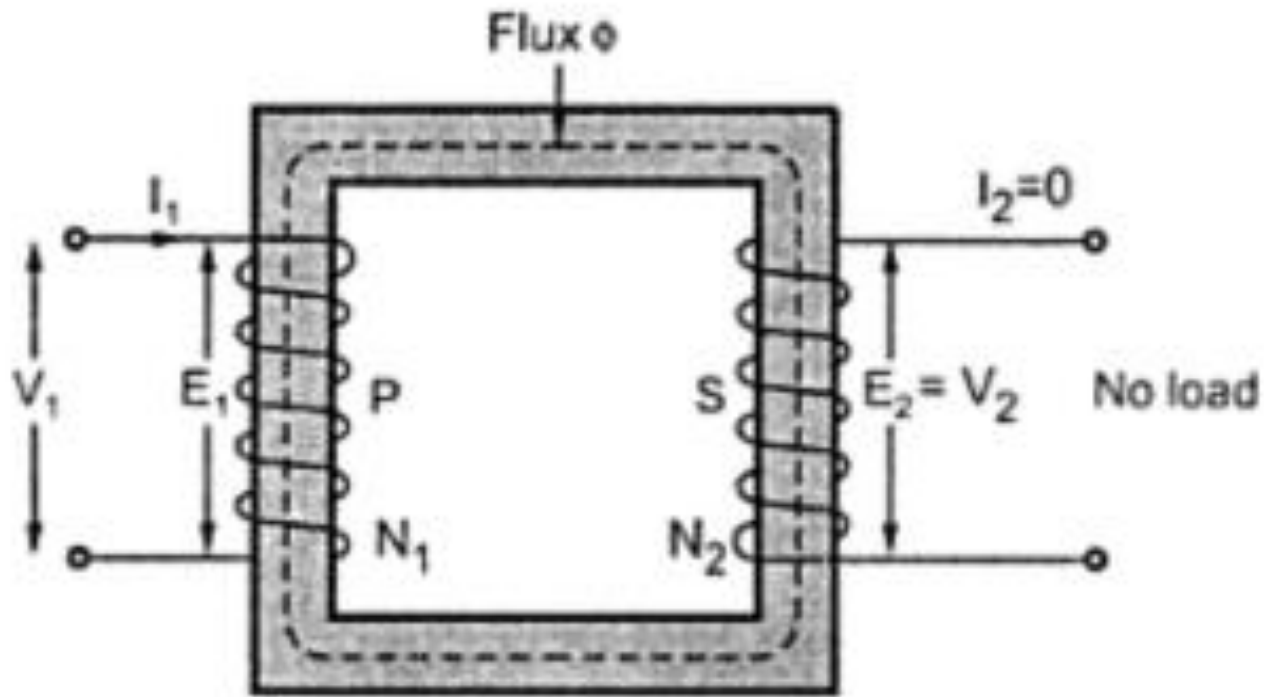

$V_1$  – supply voltage ;

$V_2$  – output voltage;

$I_m$  – magnetising current;

$E_1$  – self induced emf ;

$I_1$  – no-load input current ;

$I_2$  – output current

$E_2$  – mutually induced emf

# EMF equation of a transformer

---

## EMF equation of the Transformer

Let,

$N_1$  = Number of turns in primary winding

$N_2$  = Number of turns in secondary winding

$\Phi_m$  = Maximum flux in the core (in Wb) = ( $B_m \times A$ )

f = frequency of the AC supply (in Hz)



# EMF equation of a transformer

---

As, shown in the fig., the flux rises sinusoidally to its maximum value  $\Phi_m$  from 0. It reaches to the maximum value in one quarter of the cycle i.e in  $T/4$  sec (where,  $T$  is time period of the sin wave of the supply =  $1/f$ ).

Therefore,

$$\text{average rate of change of flux} = \Phi_m / (T/4) = \Phi_m / (1/4f)$$

Therefore,

$$\text{average rate of change of flux} = 4f \Phi_m \dots\dots (\text{Wb/s}).$$

Now,

Induced emf per turn = rate of change of flux per turn

$$\text{Therefore, average emf per turn} = 4f \Phi_m \dots\dots\dots(\text{Volts}).$$

# EMF equation of a transformer

---

Now, we know, Form factor = RMS value / average value

Therefore, RMS value of emf per turn = Form factor X average emf per turn.

As, the flux  $\Phi$  varies sinusoidally, form factor of a sine wave is 1.11

Therefore, RMS value of emf per turn =  $1.11 \times 4f \Phi_m = 4.44f \Phi_m$ .

RMS value of induced emf in whole primary winding ( $E_1$ ) = RMS value of emf per turn X Number of turns in primary winding

$$E_1 = 4.44f N_1 \Phi_m \quad \dots\dots\dots \text{eq 1}$$

# EMF equation of a transformer

---

Similarly, RMS induced emf in secondary winding ( $E_2$ ) can be given as

$$E_2 = 4.44f N_2 \Phi_m. \quad \dots\dots\dots \text{eq 2}$$

from the above equations 1 and 2,

This is called the **emf equation of transformer**, which shows, emf / number of turns is same for both primary and secondary winding.

For an [ideal transformer](#) on no load,  $E_1 = V_1$  and  $E_2 = V_2$  .

where,  $V_1$  = supply voltage of primary winding

$V_2$  = terminal voltage of secondary winding

# All day efficiency

---

$$\text{ordinary commercial efficiency} = \frac{\text{out put in watts}}{\text{input in watts}}$$

$$\eta_{all\ day} = \frac{\text{output in kWh}}{\text{Input in kWh}} \text{ (for 24 hours)}$$

- All day efficiency is always less than the commercial efficiency

# Assignment:

---

- 1) Define transformers and explain working and construction of single phase transformers?
- 2) What is Ideal Transformers?

For any Query pl Contact: Ms Richa Dubey (9998037615)  
[richa.dubey@sriict.in](mailto:richa.dubey@sriict.in)